

## UART

→ Universal Asynchronous  
Receiver & Transmitter

\* UART is much much slower than USB  
but its simple & many  
peripherals or sensors actually use it.

\* both of them do not share any common clock  
they just agree upon no. of bits,  
parity ...

Sampling =  $16 \times$  Baud rate

→ rate at which it is polling

## Oversampling



1. wait until incoming signal becomes 0

start bit), then start the sampling tick counter.

2. When tick counter reaches 7 (middle of start bit), clear tick counter & reset!


3. When counter reaches 15 (middle of first data bit), shift bit value into register & reset tick counter.


4. Repeat step 3 (N+1) times to retrieve the remaining data bits.

5. If optional parity bit is used, repeat step 3 one time more.

6. Repeat step 3

## UART Construction

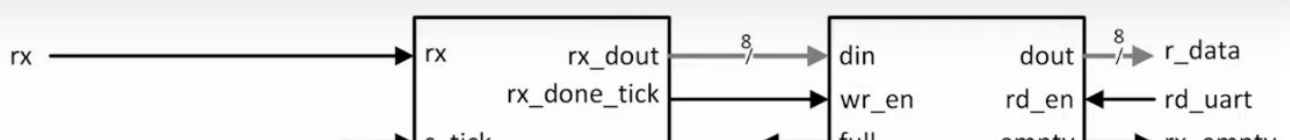

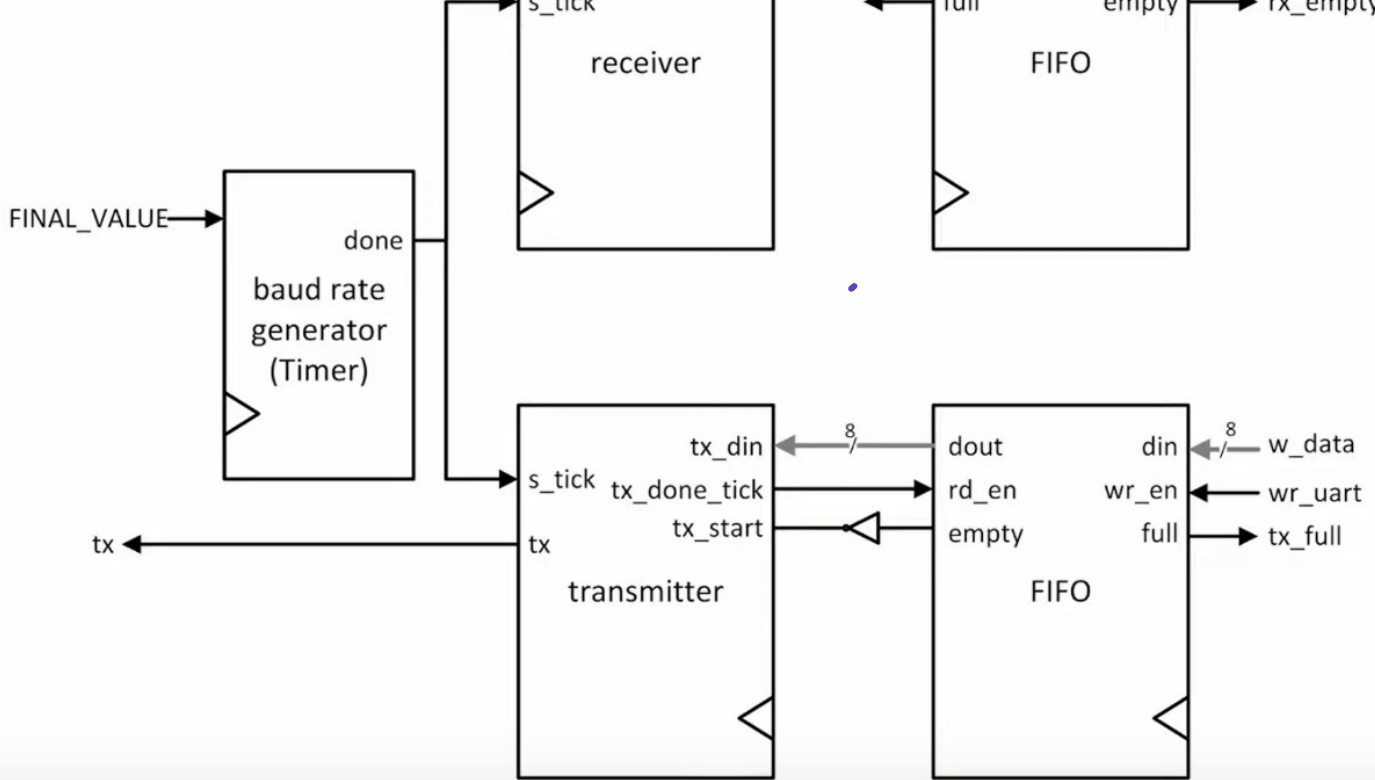

① Baud rate generator: it just ticks every certain period of time based on baud rate.


- ticks  $16 \times$  baud rate.

- it's like a timer

② Receiver is receiving at UART rate which is slower than transmitter rate which is connected to processor

Baud Rate Generator

## ↳ Calculations

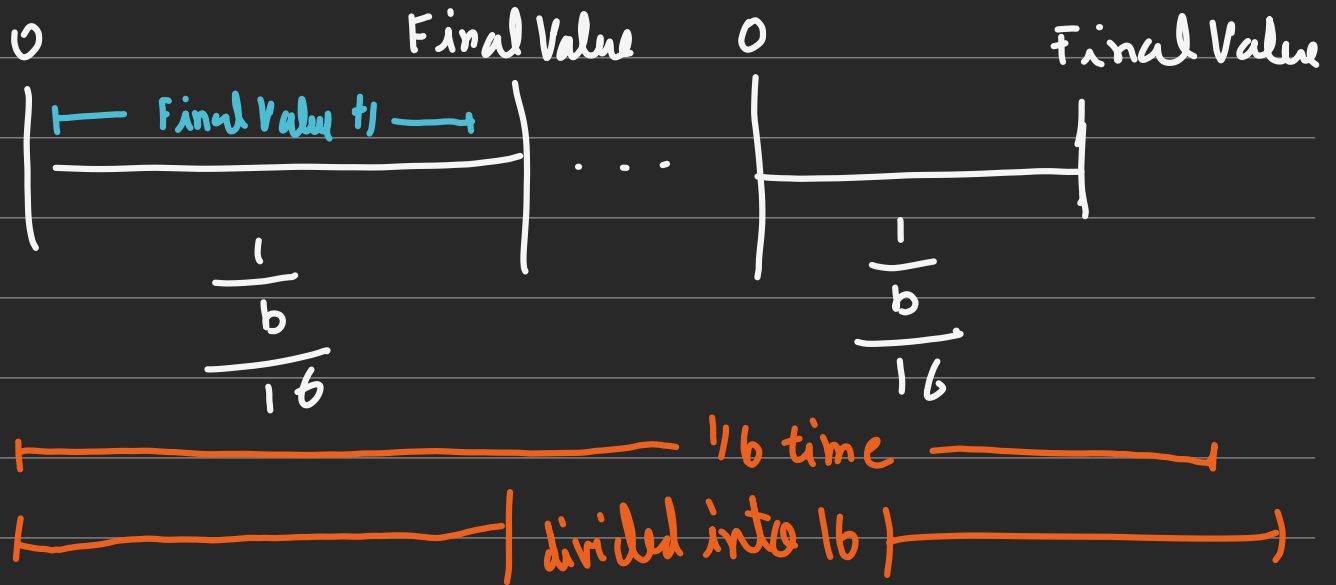

$$(Final\ Value + 1) \times T = \frac{1}{16 \times b}$$

system clock cycle

$$\Rightarrow Final\ Value = \frac{1}{16 \times b \times T} - 1$$


rate at which we transmit the data.

Ex  $f = 100\text{ MHz}, b = 9600\text{ bits/sec.}$

$$\text{then Final value} = \frac{100 \times 10^6}{16 \times 9600 \times 2} - 1$$

$$\approx 650$$

# Receiver

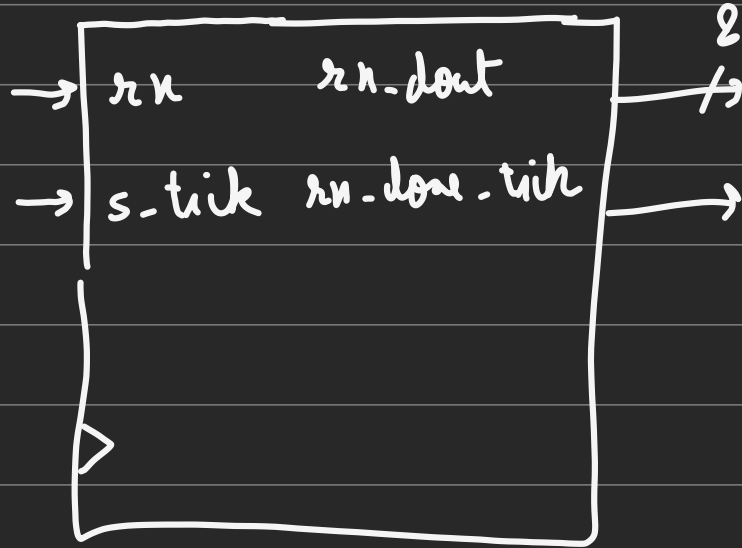

data  
↑

ASMD

