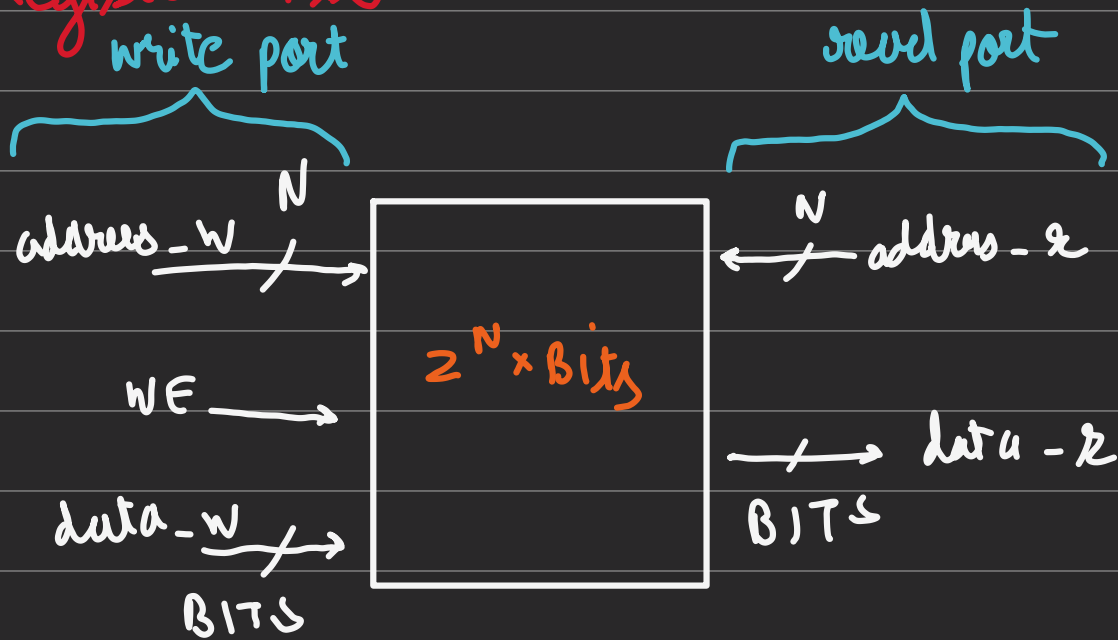


Memory Swapper


① Register File




2^N - rows
BITS - column

* Register are nothing more than bunch of FF

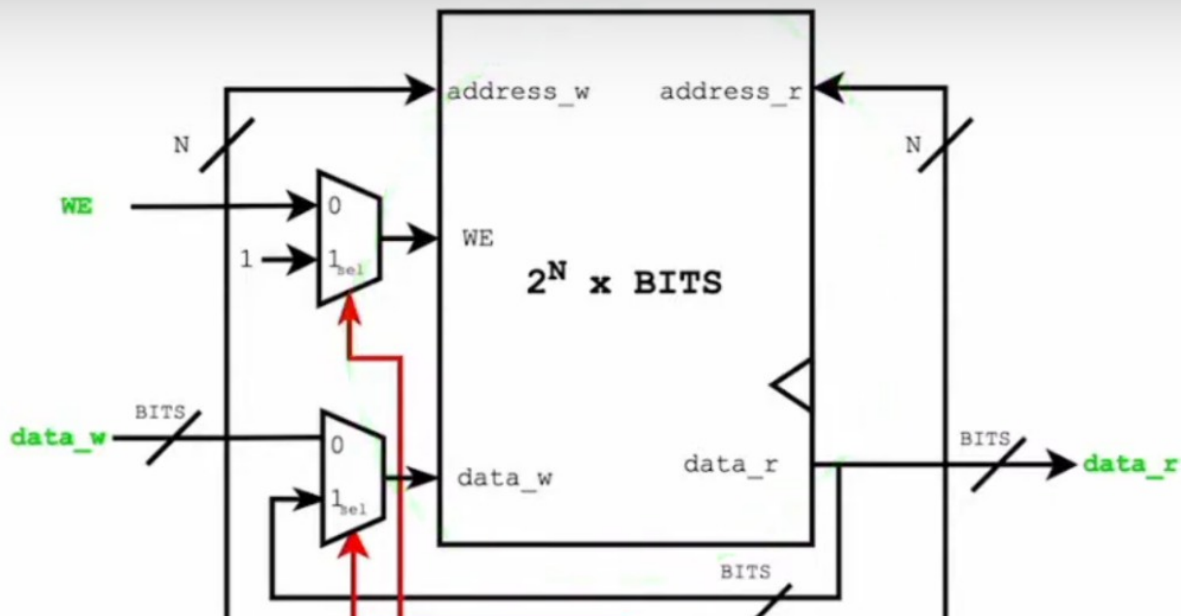→ write is synchronous & read is asynchronous : both ports are indep.



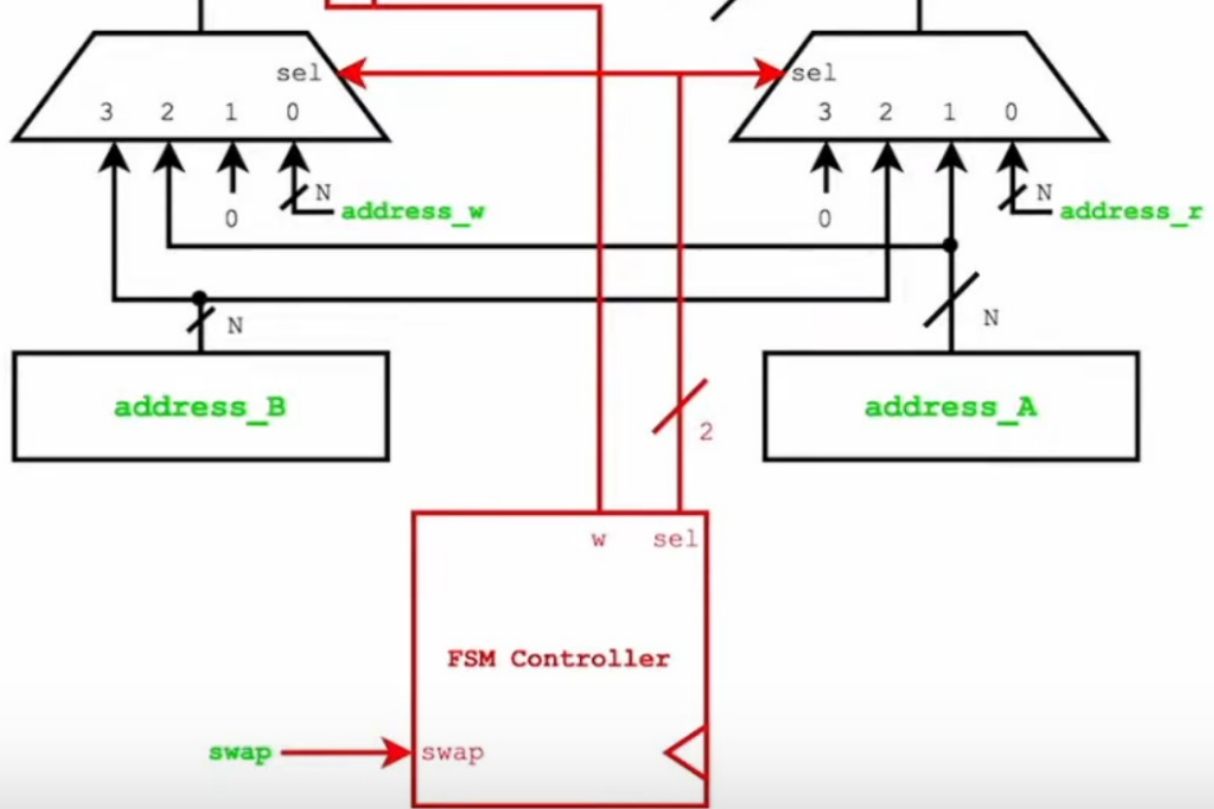

- idle
- store * A $\rightarrow$ 0x $\phi\phi$
- copy * B $\rightarrow$ & A
- copy * $\phi\phi \rightarrow$ & B

